



Category: Integrators

**CIRCUIT IDEAS FOR DESIGNERS**

Schematic no. int\_42004.0

**Inverting Switched Capacitor Integrator****Description**

This circuit charges and discharges sampling capacitor  $C_s$  by alternately switching it between input  $V_{IN}$  and the inverting terminal of the operational amplifier configured as an integrator. Frequency input is provided by digital inputs  $V_A$  and  $V_B$ , which are out-of-phase non-overlapping digital clocks. Initially  $C_s$  is charged by  $V_{IN}$ , which is connected to  $C_s$  through the analog switch and enabled by  $V_A$  (CLOSED). Next,  $V_{IN}$  is disconnected from  $C_s$  when  $V_A$  disables (open) the analog switch.  $V_B$  then enable  $C_s$  to be switched across the input terminals of the integrating amplifier.  $V_{OUT}$  is determined by the amount of charge on  $C_s$  transferred across to the integration capacitor  $C_f$ . It is important to select an analog switch that has very low charge injection specifications, such as the ALD4201. Switching by analog switch introduces charge injection that adds or subtracts extraneous charge to  $C_s$  and introduces errors to the signal charge stored on it. Clocks  $V_A$  and  $V_B$  required to drive a quad analog switch such as the ALD4201 can also be replaced with a single clock driving an ALD4213 quad analog switch. The integration current  $I_{IN}$  produced by input  $V_{IN}$  is proportional to it, given by  $I_{IN} = V_{IN}/R = V_{OUT} \times C_s \times f$ , where  $f$  is the switching clock frequency of  $V_A$  and  $V_B$ . The feedback integration capacitor  $C_f$  is charged with this integration current. The time required in charging the integrating capacitor depends directly on the magnitude of  $1/V_{IN}$  and is directly proportional to the product of  $R$  ( $R = k \times 1/f$ ) and  $C_s$ . Select an operational amplifier with a) extremely low input leakage current b) low input offset voltage c) sufficient slew rate and output current to charge the  $C_f$ .

For full schematic diagram and notes, please register and login at [aldinc.com](http://aldinc.com)