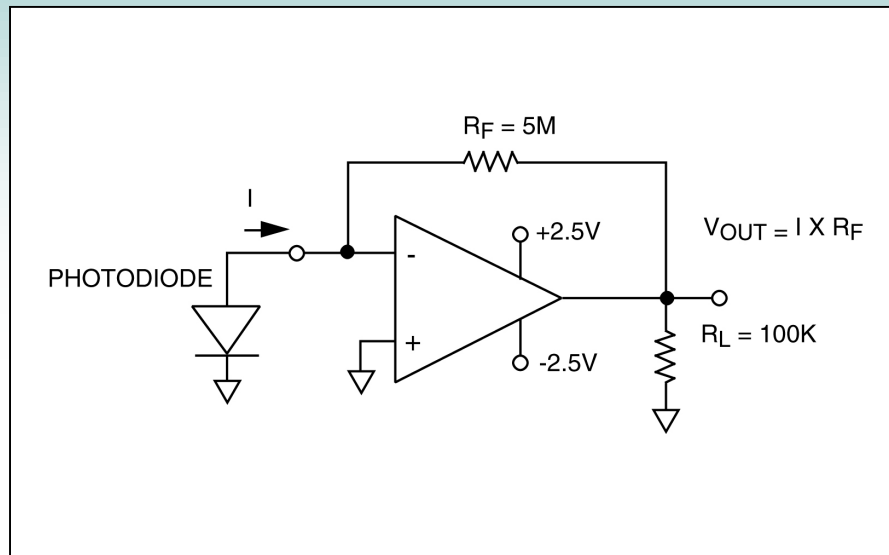




**High Precision Current to Voltage Converter**



**Description**

Net current generated by the photodiode ( $I$ ) is forced through feedback resistor ( $R_F$ ), assuming zero leakage current through the input of the buffer amplifier. This develops an output voltage equal to ( $I \times R_F$ ) at the output of the amplifier. In this example, the output also drives a load  $R_L$  of  $100K\Omega$ . Some of the errors produced by this circuit are the amplifier input-leakage current, typically about 1 to  $10pA$ , and the input offset voltage, typically about 1 to  $5mV$ . If it is important to minimize these errors, use an EPAD® op amp such as ALD1722, which has a maximum input current of  $10pA$  and maximum input offset voltage of only  $90\mu V$ .

**Recommended Components**

ALD1721, ALD2721 (dual), ALD1722, ALD2722 (dual), ALD1726, ALD2726 (dual)

**Other Related Circuit Ideas**