



Category: Oscillators

CIRCUIT IDEAS FOR DESIGNERS

Schematic no. osc_42008.0

Nanopower LC (Colpitts) Oscillator Circuit

Description

This is an ultra low-voltage LC (Colpitts) oscillator circuit using EPAD MOSFETs with passive resistor load and output buffer operating on a single 0.17V power supply. This circuit is similar in configuration to a classic LC oscillator circuit in 5V circuits. A dual EPAD MOSFET is connected in parallel to provide more low voltage drive current as necessary. The output buffer is powered by R_{OUT} , which can be selected to optimize the output voltage swing levels as well as providing adequate output drive currents.

Some performance figures: $V_+ = 0.17V$, $I_+ = 5\mu A$, $P_D = 800nW$, Crystal frequency = 1 MHz.

V_L is an output voltage level that can be equal to, higher than or lower than V_+ , depending on desired output voltage swing levels. R_{OUT} must be selected for a selected V_L and at the same time minimize current drain. An example: $V_L = 0.1V$, $I_L = 17\mu A$, $P_d = 1.7\mu W$, $V_{OH} = 59mV$, $V_{OL} = 48mV$.

For full schematic diagram and notes, please register and login at aldinc.com