

Category: SABFET CIRCUIT IDEAS FOR DESIGNERS

Schematic no. sabfet_11108.0

Balancing 2-Supercap Stack with SAB MOSFETs in Parallel

Description

Two supercapacitor auto balancing (SAB) MOSFET array connect in parallel across each supercap of a 2-supercap stack, using a quad ALD 8100xx series, with xx equal to the threshold voltage, V_t , in 0.10V increments. At V_t , the I_{DS} ON current for each of M1/M2/M3/M4 is set at 1µA. The I_{DS} ON current of M1/M2/M3/M4 change exponentially with slight changes in the gate-source voltage, V_{GS} . Each SAB MOSFET M_X behaves like a voltage sensitive resistor (See sabfet_11101.0). At V_{GS} voltages below or above V_t , the SAB MOSFET I_{DS} ON current changes at a rate of approximately 1 decade for every 0.1V change in V_{GS} . When V_{GS} drops low enough, the I_{DS} ON current becomes essentially zero. For example, the ALD810023 has a V_t of 2.30V. If its V_{GS} voltage falls below 1.7V, the I_{DS} current decreases to pA range, which is near zero compared to 1µA. Connecting two SAB MOSFETs in parallel generally means that two gates, two drains, and two sources are tied together to form a single gate, drain, and source with twice the current running through it. While this increases the leakage current at the standard operating voltage, this configuration increases the maximum charge balancing leakage current at the maximum voltage across the chosen SAB MOSFET.

The voltages across M1/M2 automatically self-adjust to accommodate different leakage currents through C1 and the voltages across M3/M4 automatically self-adjust to accommodate different leakage currents through C2. V_1 settles to approximately $\frac{1}{2}$ (V+), depending upon relative leakage currents of C1 or C2. The currents through M1/M2/M3/M4 automatically compensate for different supercap voltages. A higher supercap voltage results in a higher corresponding V_{GS} voltage of M_X connected across it, at a higher I_{DS} ON current, which opposes the tendency for the higher supercap voltage to increase. A lower supercap voltage results in lower I_{DS} ON currents in the corresponding SAB MOSFET until I_{DS} ON \approx 0. In equilibrium, the total leakage current across both M1/M2/M3/M4 and C1/C2 of each network is approximately equal to the highest leakage current of any one of C1/C2.

For full schematic diagram and notes, please register and login at aldinc.com

©2013 Advanced Linear Devices, Inc. Information furnished by Advanced Linear Devices, Inc. (ALD) is believed to be accurate and reliable. However, ALD assumes no responsibility for the use of such information nor for any infringement of patent or rights of third parties that may result from its use. No license is granted implication or otherwise under any patent rights of ALD.